

# Introduction to Digital Logic Design Lab

## EECS 31L

### Lab 5: RISK-V Single Cycle Processor


Ashley Yu

13704695

Mar 13 2022
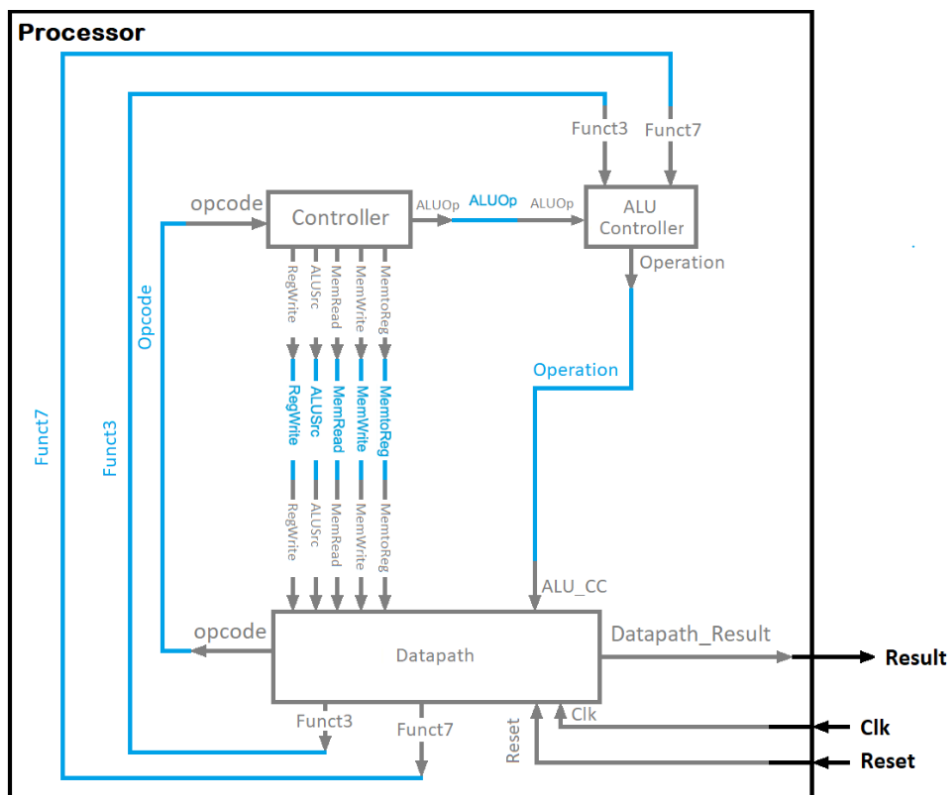
## 1. Objective


The single cycle processor takes in Clk, Reset, and outputs Result.



## 1.1 Low Level Module

 
### 1.1.1 Controller

The controller takes a opcode as input and outputs RegWrite, ALUSrc, MemRead, MemWrite, MemtoReg, and ALUOp. If opcode is the Load instruction, MemWrite is set to 0 while everything else is 1. If it is the Store instruction, MemWrite and ALUSrc are set to 1 while the other three are 0. In both Store and Load, the ALUOp is 01. If it is the case of “0010011” then ALUSrc and RegWrite are 1 while the rest are 0 and ALUOp is 00. Lastly, when it is “0110011” RegWrite is 1 with all others being 0 and ALUOp as 10.


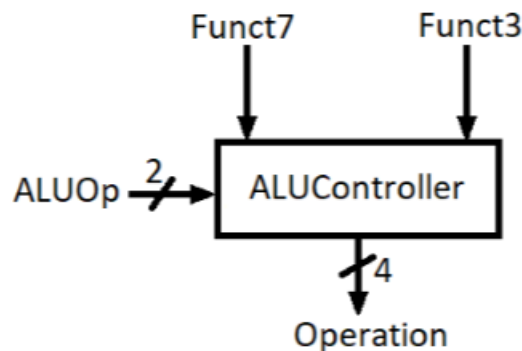
### 1.1.2 ALUController


The ALU Controller takes in 2 bit ALUOp, Funct7, and Funct3 as inputs when it outputs a 4 bit Operation. It decides which operation the ALU should perform based on the values of the three inputs.


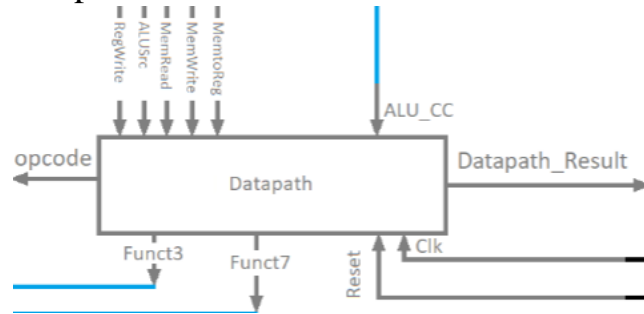
### 1.1.3 Datapath

Datapath takes in the five outputs of MemtoReg, ALUSrc, RegWrite, MemRead, and Memread from the Controller, ALU\_CC or Operation from the ALUController, and the Clk and Reset as inputs when it outputs the opcode, funct3, and


funct7 to the Controller and ALUController and the Datapath\_Result out as Result.



## 1.2 Higher Level Module
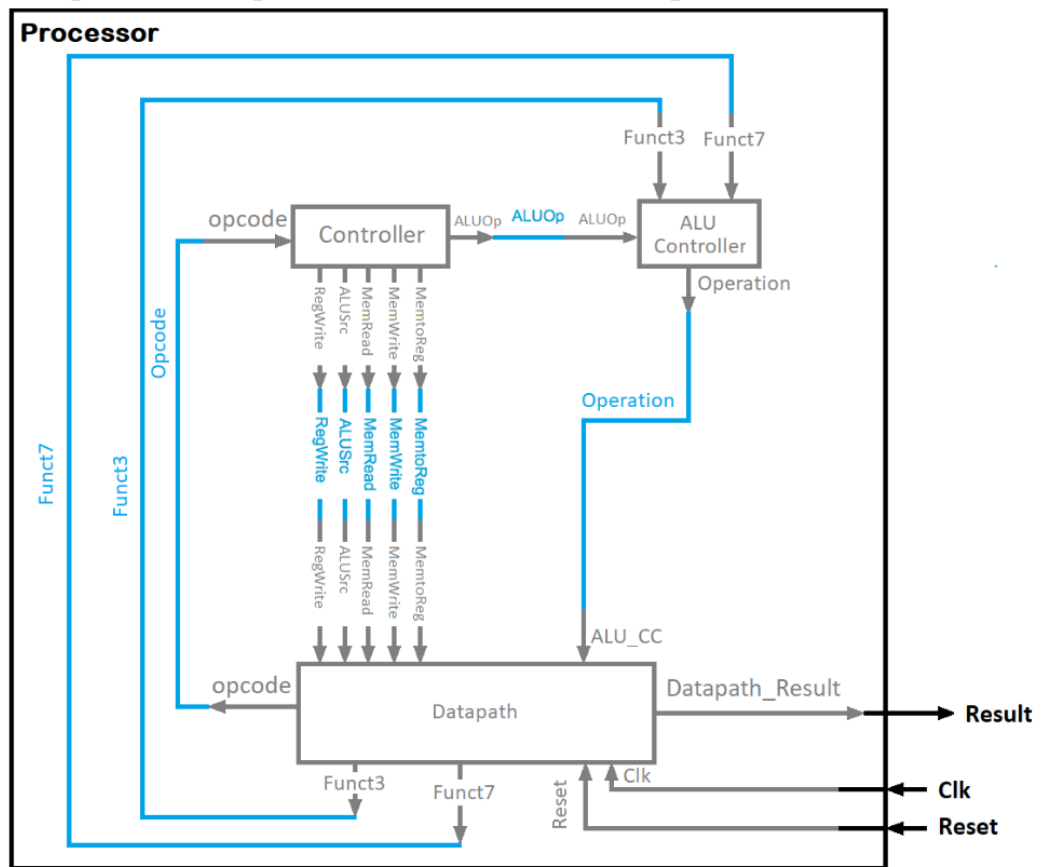
### 1.2.1 Processor

The processor inputs Clk and reset while output Result.



## 2. Procedure

### 2.1 Low Level Module

#### 2.1.2 2.1.1 Controller

I used the design block diagram from the Overview section and this truth table for the Controller.

Table 2 : Control Signals.

		Opcode			
		0110011	0010011	0000011	0100011
		AND, OR, ADD, SUB, SLT, NOR	ANDI, ORI, ADDI, SLTI, NORI	LW	SW
Control Signals	MemtoReg	0	0	1	0
	MemWrite	0	0	0	1
	MemRead	0	0	1	0
	ALUSrc	0	1	1	1
	Regwrite	1	1	1	0
	ALUOp	10	00	01	01

### 2.1.2 ALUController

I used this truth table and the design block diagram from the Overview section to create this ALUController.

Table 4 : The truth table for the 4 operation code.

	Funct7	Funct3	ALUop	Operation			
AND	0000000	111	10	0	0	0	0
OR	0000000	110	10	0	0	0	1
NOR	0000000	100	10	1	1	0	0
SLT	0000000	010	10	0	1	1	1
ADD	0000000	000	10	0	0	1	0
SUB	0100000	000	10	0	1	1	0
ANDI	-	111	00	0	0	0	0
ORI	-	110	00	0	0	0	1
NORI	-	100	00	1	1	0	0
SLTI	-	010	00	0	1	1	1
ADDI	-	000	00	0	0	1	0
LW	-	010	01	0	0	1	0
SW	-	010	01	0	0	1	0

### 2.1.3 Datapath

I used this code and the design block diagram from the Overview section to create this instruction memory.

```

`timescale 1ns / 1ps
module data_path #(
parameter PC_W = 8, // Program Counter
parameter INS_W = 32, // Instruction Width
parameter RF_ADDRESS = 5, // Register File Address
parameter DATA_W = 32, // Data WriteData
parameter DM_ADDRESS = 9, // Data Memory Address
parameter ALU_CC_W = 4 // ALU Control Code Width
) (
input clk ,
input reset ,
input reg_write ,
input mem2reg ,
input alu_src ,
input mem_write ,
input mem_read ,
input [ALU_CC_W -1:0] alu_cc ,
output [6:0] opcode ,
output [6:0] funct7 ,
output [2:0] funct3 ,
output [DATA_W -1:0] alu_result );
wire [PC_W -1:0] pc , pc_next;
wire [INS_W -1:0] instruction;
wire [DATA_W -1:0] l_alu_result;
wire [DATA_W -1:0] reg1 , reg2;
wire [DATA_W -1:0] l_read_data;
wire [DATA_W -1:0] l_reg_wr_data;
wire [DATA_W -1:0] srcb ;
wire [DATA_W -1:0] extimm;
// next pc
assign pc_next = pc + 4;
FlipFlop pcreg(clk , reset , pc_next , pc);
assign pc_next = pc + 4;
FlipFlop pcreg(clk , reset , pc_next , pc);
// instruction memory
InstMem instruction_mem (pc , instruction );
assign opcode = instruction [6:0];
assign funct7 = instruction [31:25];
assign funct3 = instruction [14:12];
// register file
RegFile rf(
.clk ( clk ),
.reset ( reset ),
.rg_wrt_en ( reg_write ),
.rg_wrt_addr ( instruction [11:7] ),
.rg_rd_addr1 ( instruction [19:15] ),
.rg_rd_addr2 ( instruction [24:20] ),
.rg_wrt_data ( l_reg_wr_data ),
.rg_rd_data1 ( reg1 ),
.rg_rd_data2 ( reg2 ));
assign l_reg_wr_data = mem2reg ? l_read_data : l_alu_result;
// sign extend
ImmGen ext_imm (instruction , extimm );
// alu
assign srcb = alu_src ? extimm : reg2;
alu_32 alu_module( .A_in(reg1), .B_in(srcb), .ALU_Sel(alu_cc),
.ALU_Out(l_alu_result), .Carry_Out (), .Zero(), .Overflow ());
assign alu_result = l_alu_result;
// data memory
DataMem data_mem (.addr(l_alu_result[DM_ADDRESS -1:0]) , .read_data(l_read_data),
.write_data(reg2), .MemWrite(mem_write), .MemRead(mem_read) );
endmodule

```

### 3. Simulation Results

Test:

Reset is 1 from 10ns to 30ns and 0 the rest. Clk starts a 0 and turns on every 10 ns. Result is initially X like reset for the first 10ns and 0 when reset is on.

Then at every positive edge of the clock the result updates. By checking the point array I can be sure that my results are correct.

